

The City College of New York  
Grove School of Engineering  
EE 32200 – Electrical Engineering Laboratory II  
Fall 2016

**Lab Report Experiment # 4**  
**Audio Amplifier (Part 1)**

**Instructor: Ritesh Chaudhuri**

**Azizur Rahman**  
**Hasan Uchchas**

November 1, 2016

## Objective :

In this experiment we will design and build an audio amplifier circuit and then test its performance. An audio amplifier should be able to amplify its input signal without distortion.

## Pre-lab:

The first part of the pre-lab is all hand calculations; we are to find the values of resistors and voltages at specific points as well as the collector current. To make our calculations easier, we will assume that  $\beta$  is infinite, which means that there is no input base current, the source resistance is 0, which doesn't lower the input voltage, because it won't create a voltage divider at the input. The formulas that we used to calculate all the values is shown in below which is given in lab manual.

$$R_C = Z_{out}$$

$$I_C = (V_{CC} - V_{CQ}) / R_C$$

$$r_e = V_t / I_C$$

$$R_{E1} = (R_C / \text{gain}) - r_e$$

$$V_B = I_C (R_{E1} + R_{E2}) + V_{BE}$$

$$R_2 = (Z_{in} * V_{CC}) / V_B$$

$$R_1 = V_B * R_2 / (V_{CC} - V_B)$$

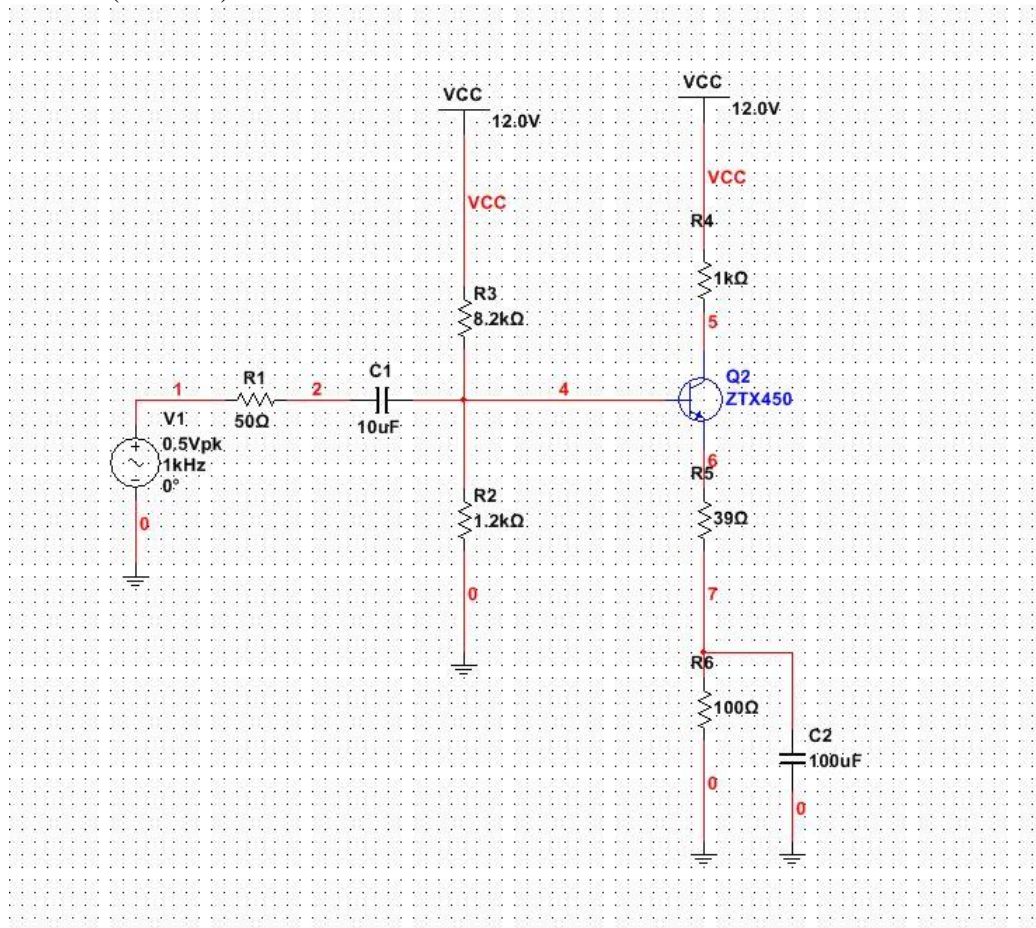


Figure1: circuit with the calculated resistor value.

| Parameter                             | Minimum | Typical | Maximum | Units           |
|---------------------------------------|---------|---------|---------|-----------------|
| V <sub>cc</sub>                       |         | 12      |         | Volts           |
| Gain                                  | 15      | 20      | 30      | V/V             |
| Z <sub>in</sub>                       | 800     | 1000    | 1200    | Ohms            |
| Z <sub>out</sub>                      | 700     | 1000    | 1200    | Ohms            |
| Maximum output swing without clipping | 7       |         |         | V <sub>pp</sub> |

| Resistor                 | Capacitor             | Quiescent Voltages and Current |
|--------------------------|-----------------------|--------------------------------|
| R <sub>1</sub> =1.2k ohm | C <sub>B</sub> =10uf  | V <sub>B</sub> =1.3            |
| R <sub>2</sub> =8.2kohm  | C <sub>E</sub> =100uf | V <sub>E</sub> =0.83           |
| R <sub>c</sub> =1k ohm   |                       | V <sub>CQ</sub> =6             |
| R <sub>E1</sub> =39 ohm  |                       | I <sub>CQ</sub> =6mA           |
| R <sub>E2</sub> =100 ohm |                       |                                |

The R<sub>c</sub> is given as Z<sub>out</sub> of the amplifier, which is typically 1kΩ. V<sub>CQ</sub> is given as the value that would give the maximum output swing, which is 6V, since the transistor has a gain of 2V/V. We will be using the typical values of the parameters to do our calculations.

I<sub>CQ</sub> is the current going through the collector of the BJT and is given as

$$I_{CQ} = \frac{V_{CC} - V_{CQ}}{R_C} = 6mA$$

r<sub>e</sub> is the impedance of the transistor and we can find it once we convert it into the small signal equivalent circuit of the BJT.

$$r_e = \frac{V_T}{I_C} = 4.17\Omega$$

As an approximation, the gain is given as the impedance looking up at the V<sub>out</sub> over the impedance looking down. Therefore,

$$Gain = R_C / (r_e + R_{E1})$$

Which can be written as

$$R_{E1} = \frac{R_C}{Gain} - r_e \approx 39\Omega.$$

V<sub>E</sub> is the voltage at the emitter and is given by

$$V_E = \frac{R_{E2} + R_{E1}}{I_C} = 0.83V$$

And V<sub>B</sub> is the voltage at the base and is given as

$$V_B = V_E + V_{BE} = 1.3V$$

Where  $V_{BE}$  is equal to 0.7V. An alternative way of finding  $V_B$  is to do a voltage divider across  $R_1$ ,

$$V_B = V_{CC} \left[ \frac{R_1}{R_1 + R_2} \right]$$

Which should give us the same answer, 1.3V.

$Z_{in}$  is the impedance looking into the base of the BJT and is given as

$$Z_{in} = R_1 * \frac{R_2}{R_1 + R_2}$$

We will use this equation along with the alternative equation to find  $V_B$  to find  $R_1$  and  $R_2$ , with a little manipulation, we will find that

$$\frac{V_B}{V_{CC}} = \frac{Z_{in}}{R_2}$$

$$R_2 \approx 820\Omega$$

$R_1$  is then found as follows,

$$R_1 = Z_{in} R_2 / (R_2 - Z_{in})$$

$$R_1 \approx 1.2k\Omega$$

The capacitors  $C_B$  and  $C_E$  are included in this amplifier to reduce the noise given off by the input signal source.

Computer Simulations:

We were to use standard resistor values that we acquired through our hand calculations then run DC bias point analysis using Multisim. Our design is shown in Figure 1.

From DC analysis we get the value of  $V_b(v1)$ ,  $V_c(v3)$ , and  $V_e(V4)$  is

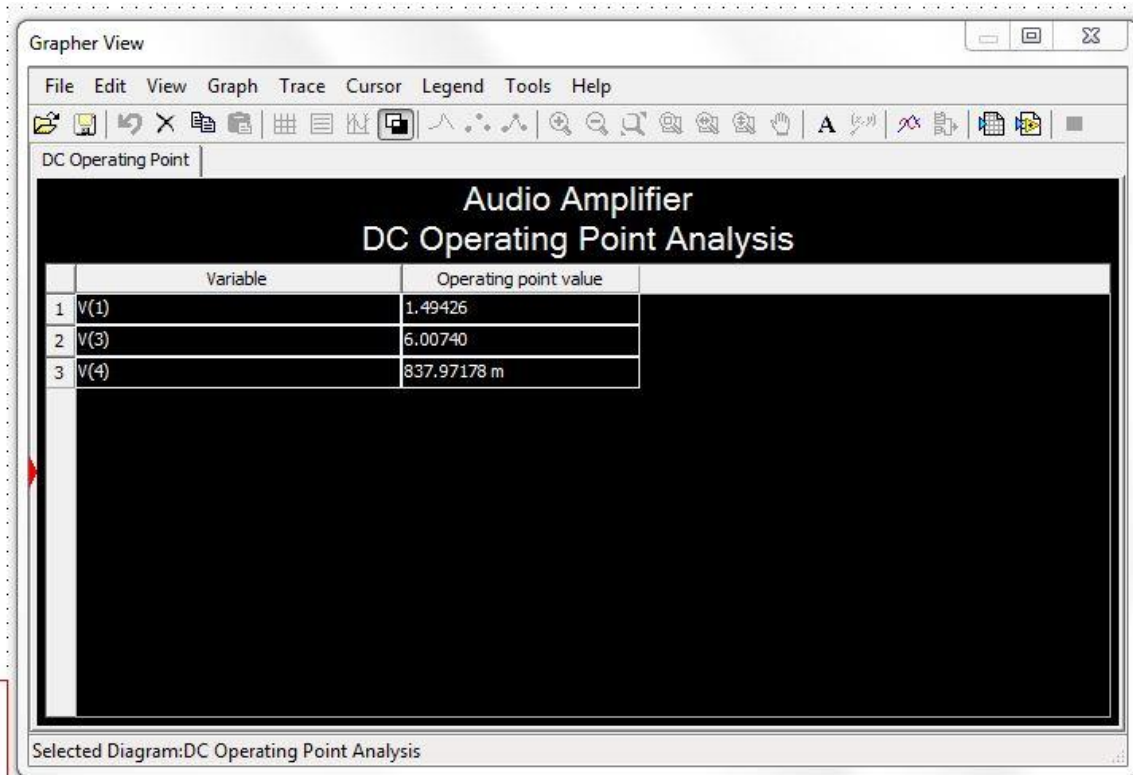


Figure: DC analysis of the figure 1.

Next, we ran a transient analysis with  $V_s$  set to 1kHz and  $R_s$  to  $50\Omega$ . Figure 2, 3, and 4 will show the different output waveforms for different voltage inputs of 50mVpp, 500mVpp, 1Vpp, respectively.

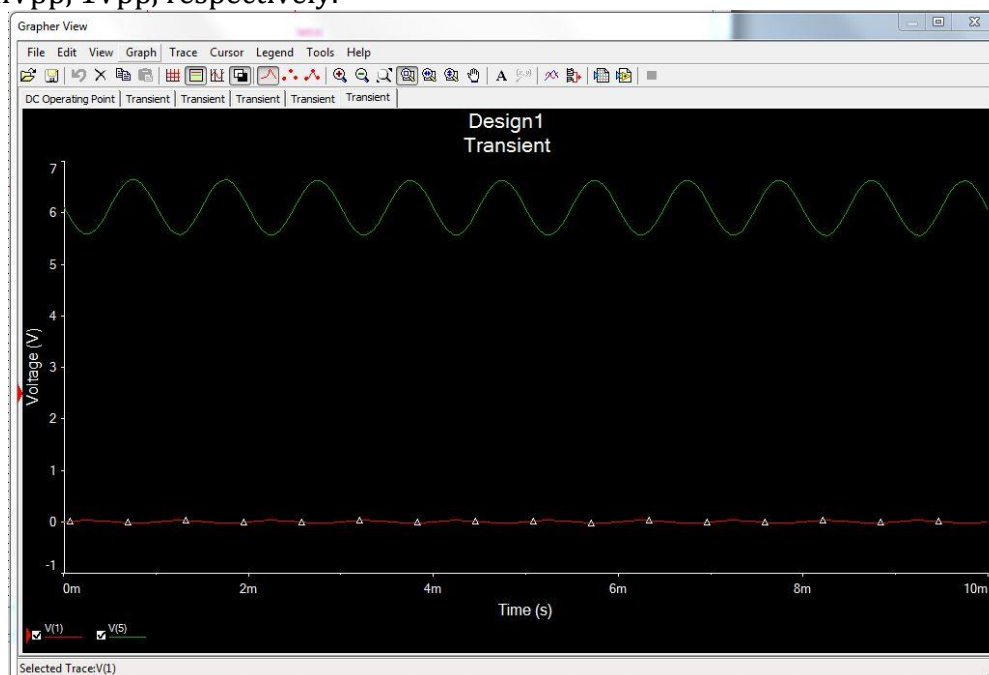


Figure: output voltage for 50mVpp input.

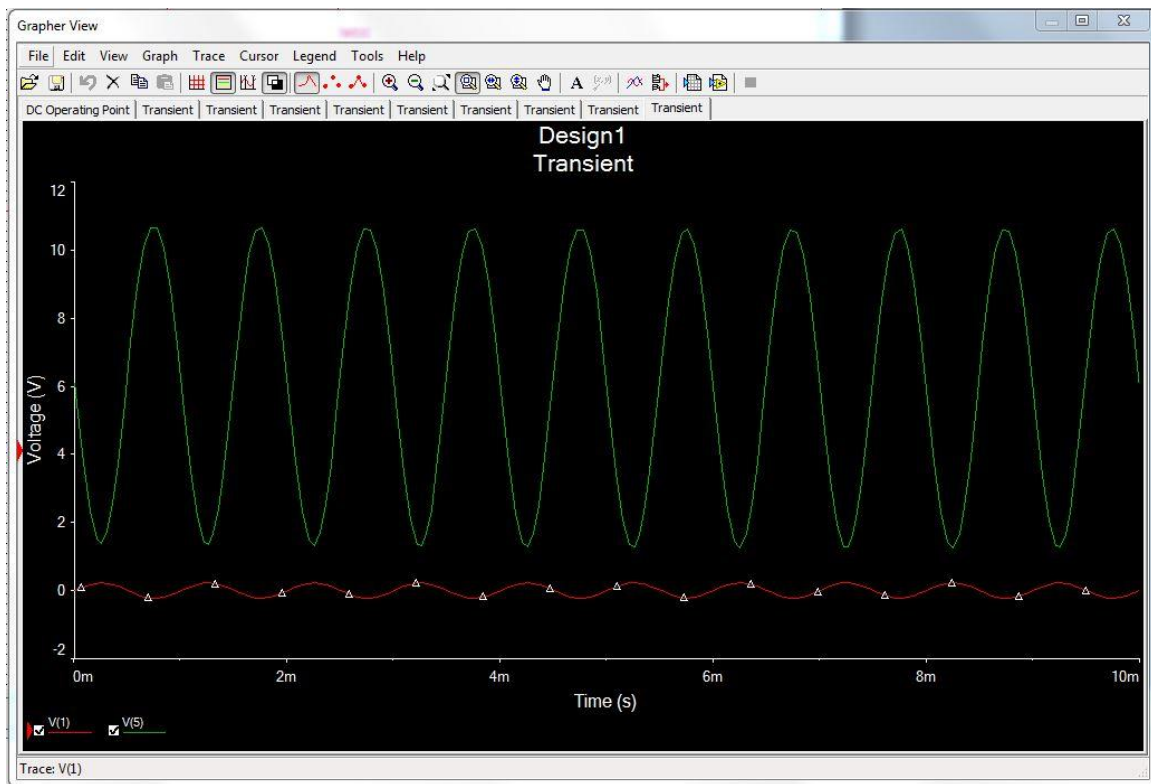


Figure: output voltage for 450mVpp input.

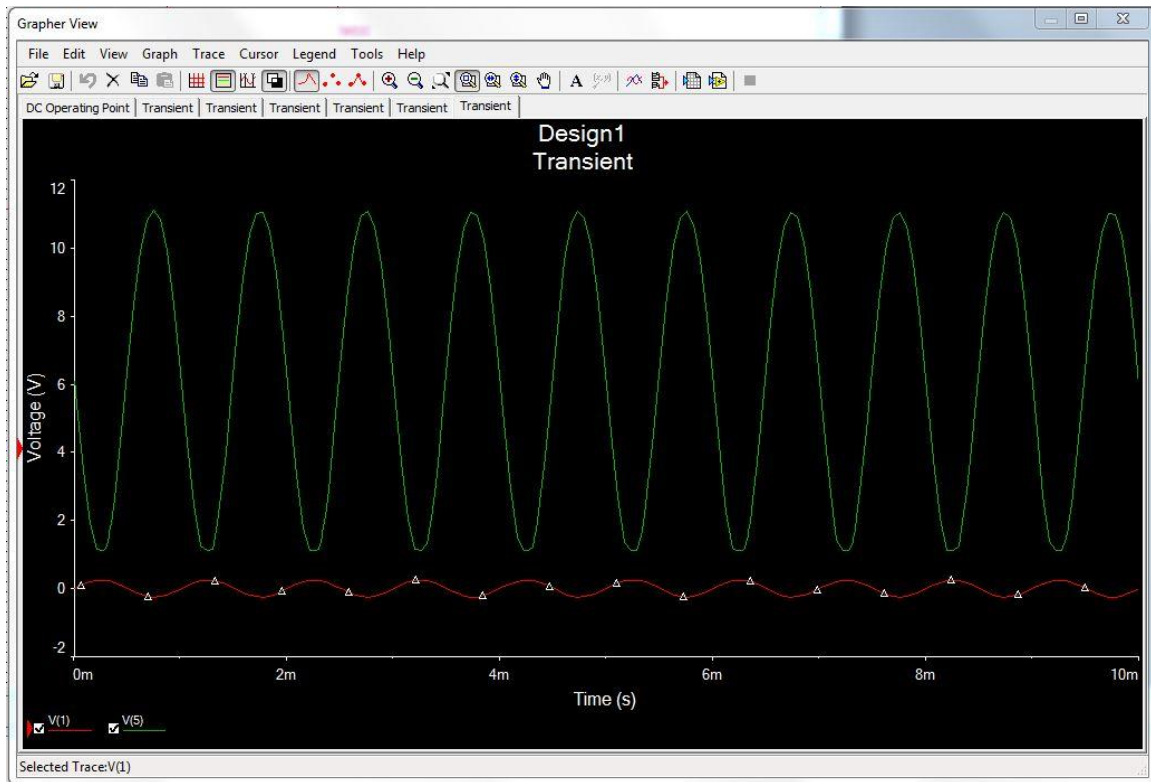


Figure: output for 500m Vpp input.

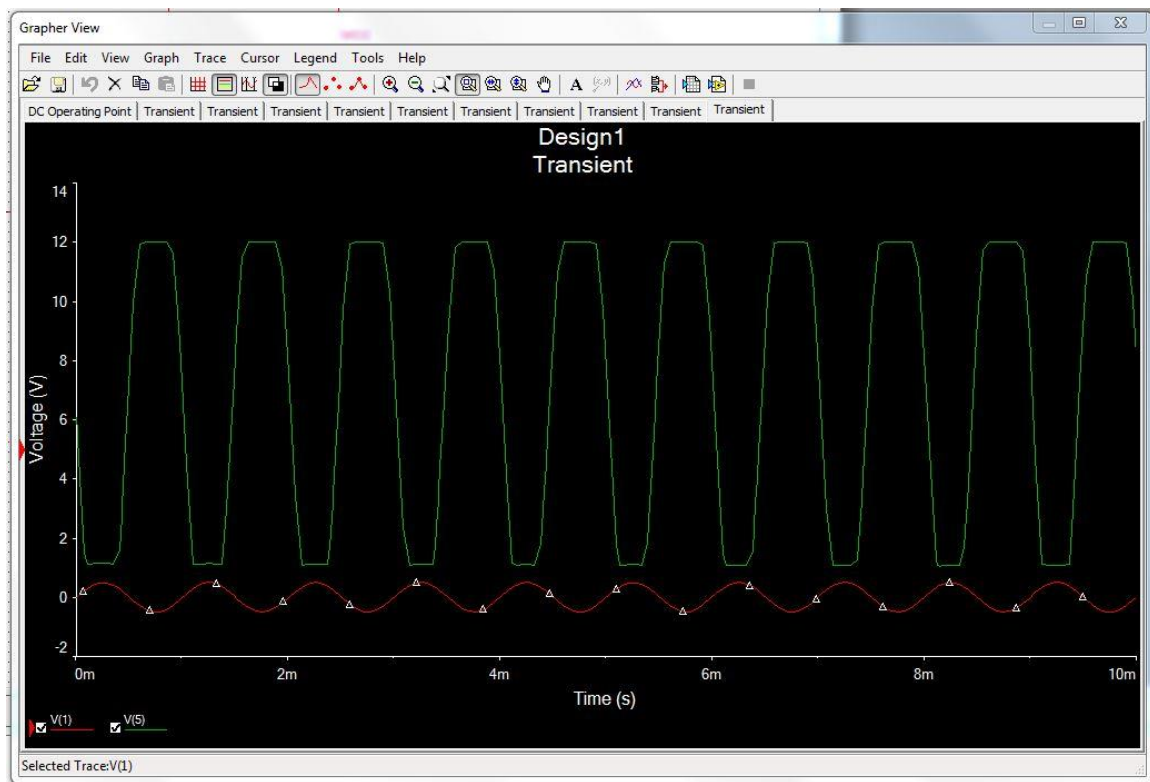


Figure: output waveform for 1 Vpp input.

As we can see, with a 50mVpp, 450mVpp and 500mVpp input, there is no distorting, however, once we have reach 1Vpp input, the output voltage is clipped on top and on the bottom. Our maximum input that does not create distortion is about 450mVpp. We obtain a gain of 9.575V/V with this input.

The reason why the plot would clip on the bottom and the top is because the amplifier is trying to amplify excessive voltage or current that is beyond its capacity.

The gain that we obtained with an input of 50mVpp is 8.63 V/V, which meets the gain specification of the table.

### Laboratory Experiment:

For the laboratory portion, we constructed the design shown in Figure 1.

We kept the wires as short as possible to minimize inductance and added a 1000 $\mu$ f capacitor to bypass the power supply. This capacitor guarantees the power supply is an AC short.

We then measured the quiescent voltages at the base, collector, and emitter. We found that

$$V_B = 1.48V$$

$$V_E = 0.852V$$

And  $V_C = 5.9V$

Our measured quiescent voltages match with our simulated quiescent voltages.

Figure 6 shows the oscilloscope image of our input and output when the function generator at 1kHz.

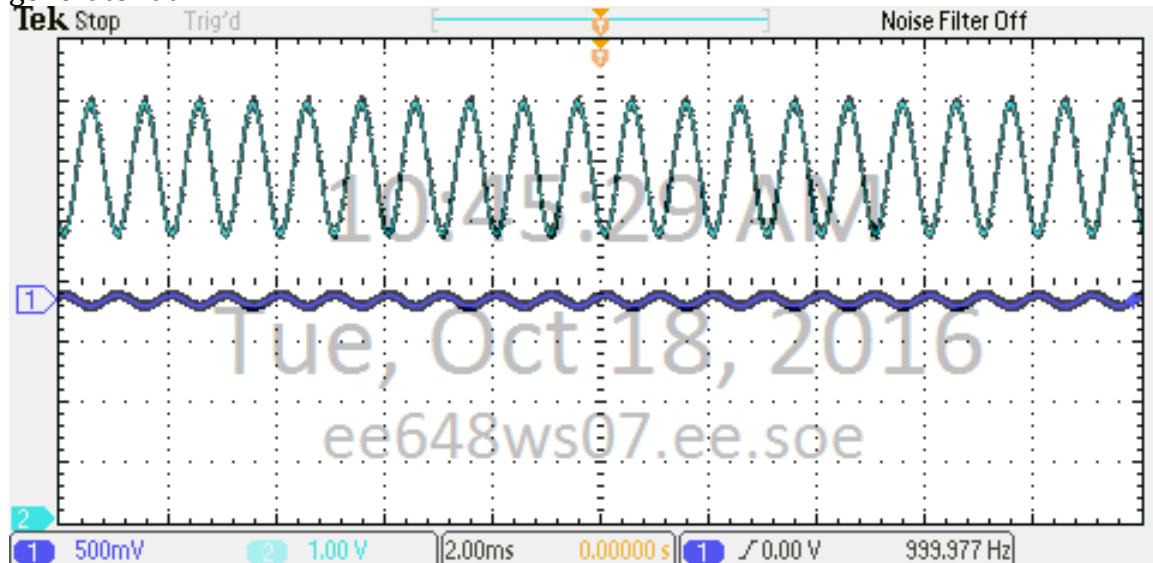


Figure: Output waveform for 1 kHz.

The gain obtained from this oscilloscope image is 16.5 V/V, which meets the specifications. The maximum undistorted output voltage swing of the amplifier was 9.2Vpp.

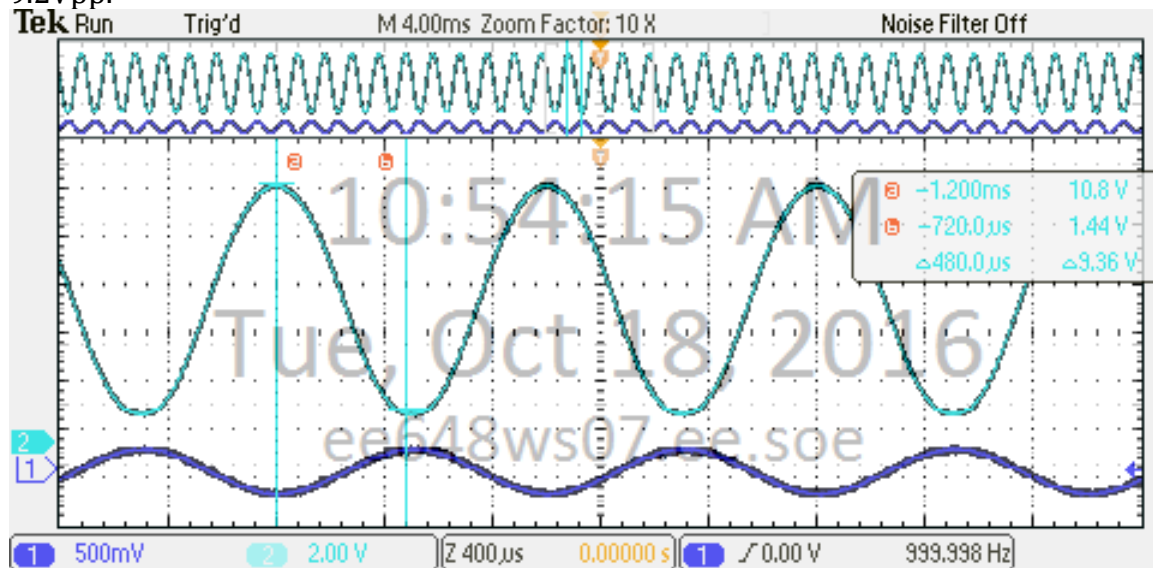


Figure: maximum undistorted output.

The maximum undistorted output voltage swing of the amplifier was 9.36Vpp, which gives us 15.09 V/V as the gain.



Next part of this laboratory is to change the different input frequencies to show when the gain would fall off or stabilize, it will be shown in the table and the Matlab Figure below.

| Frequency | Vin   | Vout  | Gain |
|-----------|-------|-------|------|
| 10Hz      | 240mv | 240mv | 1    |
| 20Hz      | 240mv | 480mv | 2    |
| 40Hz      | 240mv | 1.6V  | 6.67 |
| 70Hz      | 240mv | 4.64V | 19.3 |
| 100Hz     | 240mv | 7.12V | 29.3 |
| 150Hz     | 240mv | 8.96V | 37.3 |
| 300Hz     | 240mv | 9.28V | 38.7 |
| 600Hz     | 240mv | 9.36V | 39   |
| 1kHz      | 240mv | 9.36V | 39   |
| 3kHz      | 240mv | 9.44V | 39.3 |
| 10kHz     | 240mv | 9.44V | 39.3 |

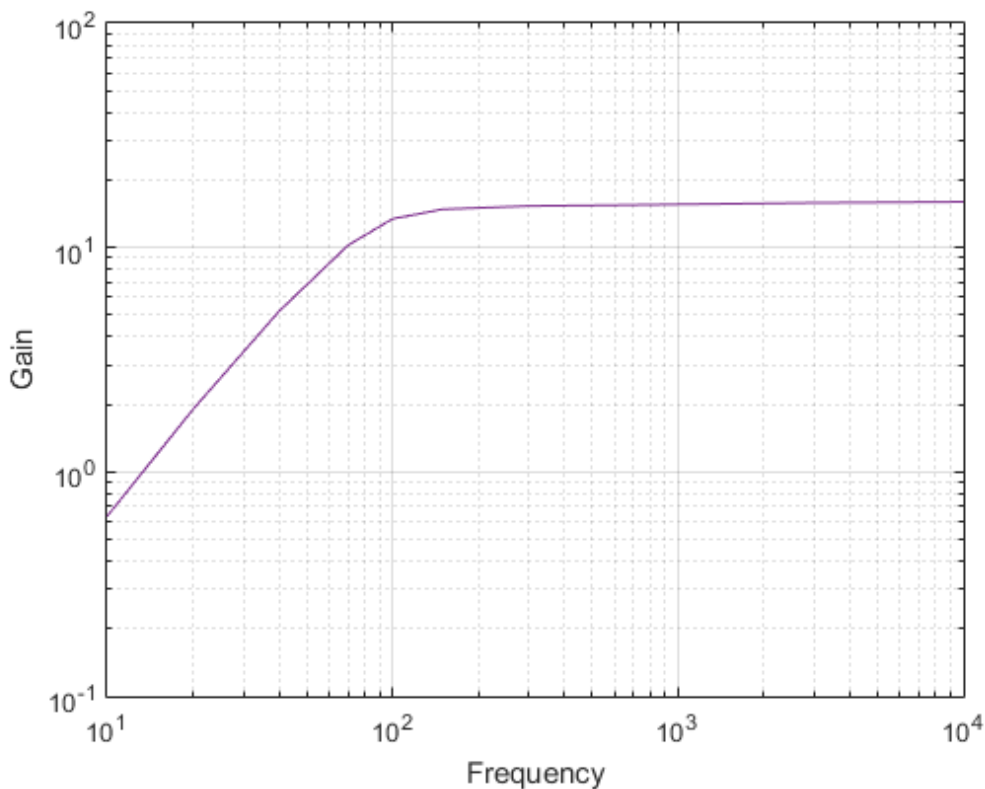


Figure: loglog plot of the table.

From Figure 8, we can see that our amplifier can only achieve a stabilized gain at high frequencies. This is because at low frequencies,  $C_B$  and  $C_E$  will no longer act as short and will contribute to the gain falling off at low frequency.

To find  $Z_{in}$  and  $Z_o$ , we find the values of  $R_S$  and  $R_{Load}$  that causes the gain to drop to half when its measured with  $R_S = 0$  and  $R_{Load} = \infty$ , respectively. The values for the resistors were  $1k\Omega$  for  $R_S$  and  $R_{Load}$ .

**Conclusion:**

Therefore, the amplifier that we constructed meets the design specifications perfectly, with the gain being  $16.5V/V$ , the  $Z_{in}$   $1k\Omega$  same as the  $Z_{out}$ , and maximum output swing  $9.36V_{pp}$ . The measured values were very close to the simulated values with a few % error, which is most likely due to the tolerance level of the resistors and the instrumental errors. Since our experiment meets the specifications, we can use this to connect to the power amplifier.