

## EE 342: Electronics II Simulation Project

By Hasan Uchchas

### Problem 1:

Through hand calculation,  $R_1$  was found to be 6.9 K. Using Multisim, through trial and error,  $R_1$  was found to be 7225 ohms. This resulted in  $V_o$  to be 0.032 V, which is within the range of the given specification.

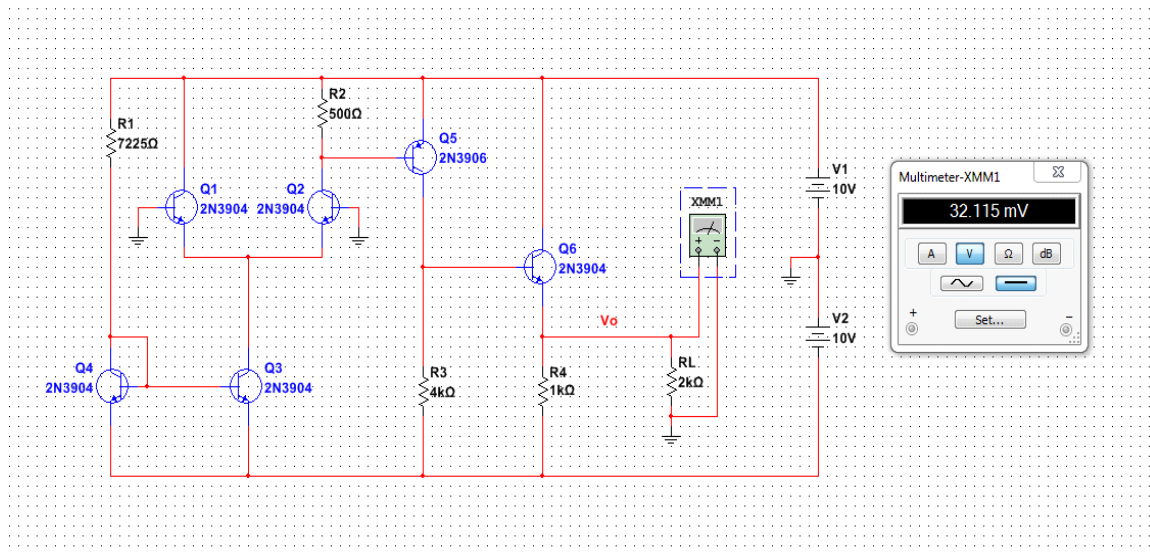


Figure 1. Finding the value of  $R_1$

### Problem 2:

The DC transfer function was plotted below. The gain is estimated to be 1800 v/v.

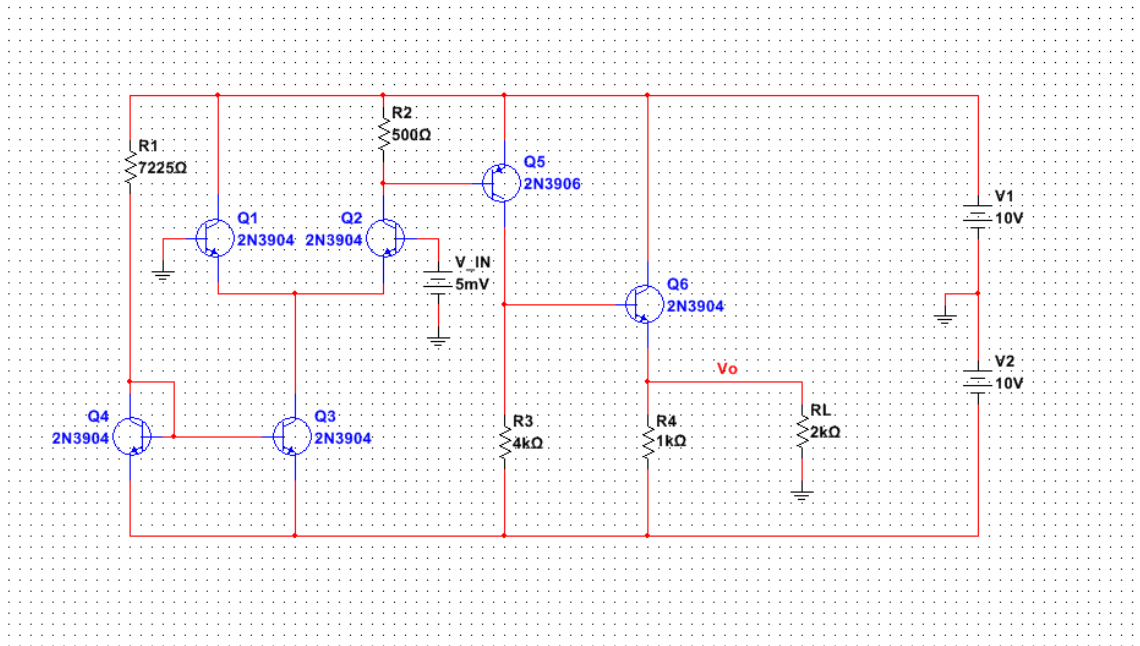


Figure 2. Finding the gain of the Op-Amp

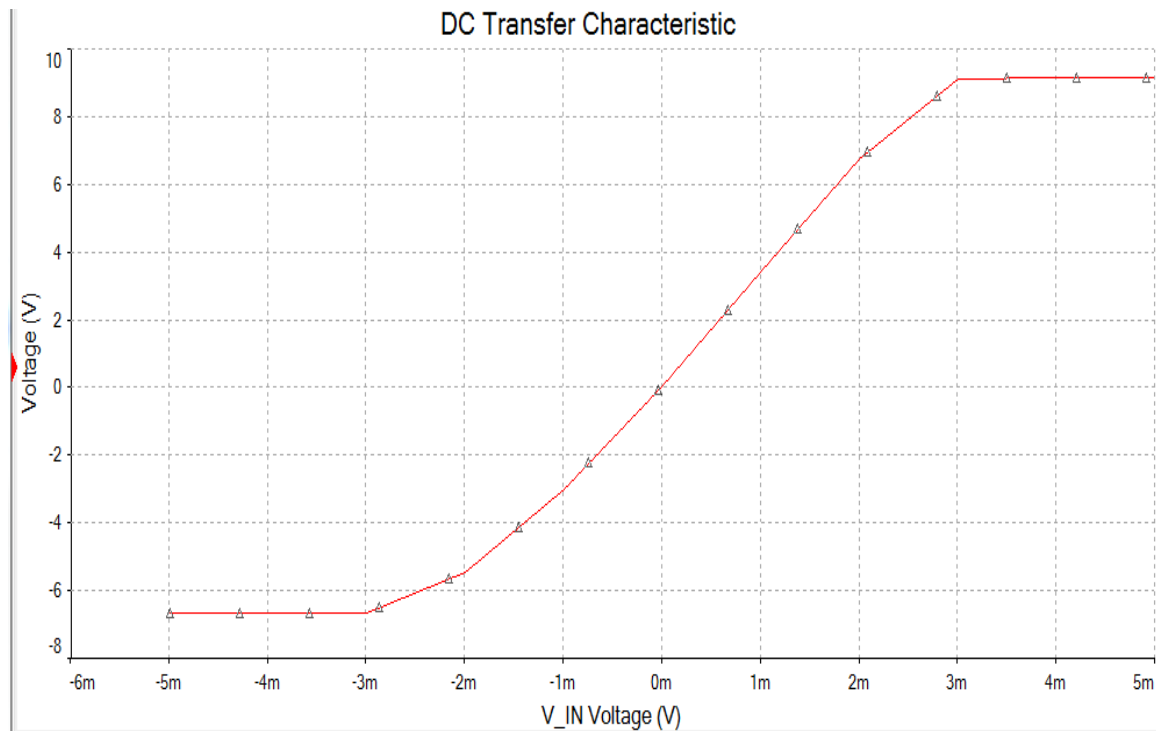


Figure 3. Plotting Vo vs. Vin

**Problem 3:** The open loop gain and the phase as a function of frequency was plotted below.

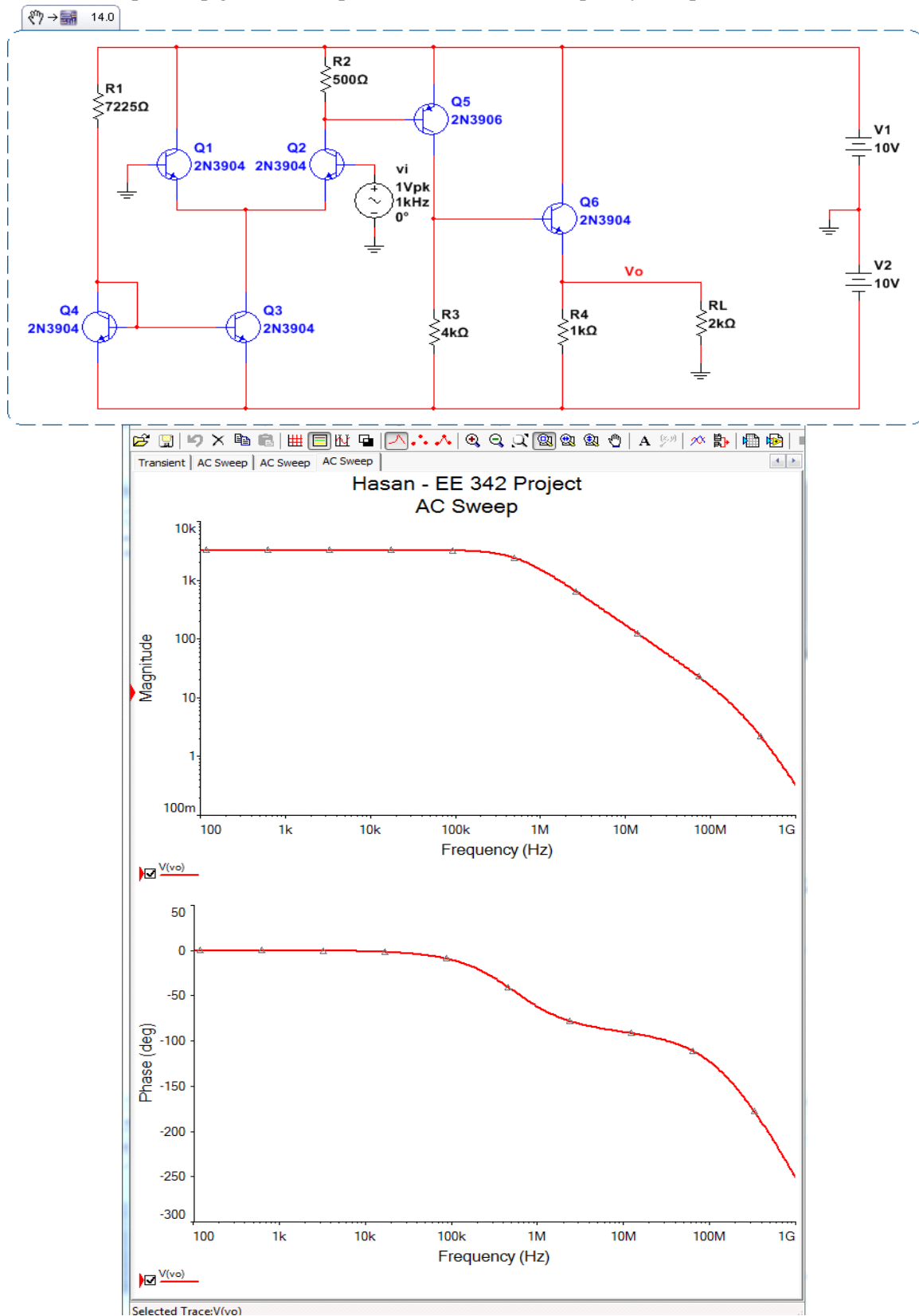


Figure 4. Plotting the open loop gain and the phase as a function of frequency

#### Problem 4: Stabilizing the Op-Amp using a compensating capacitor

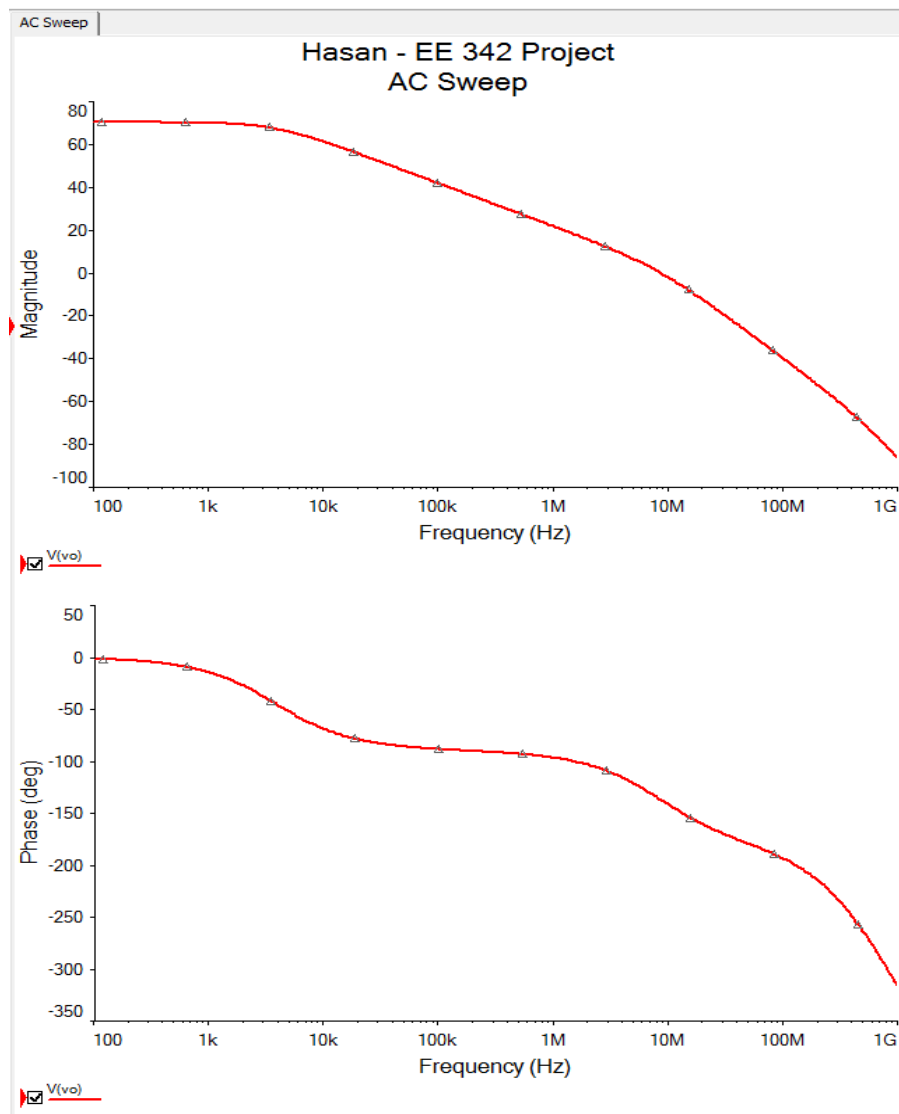
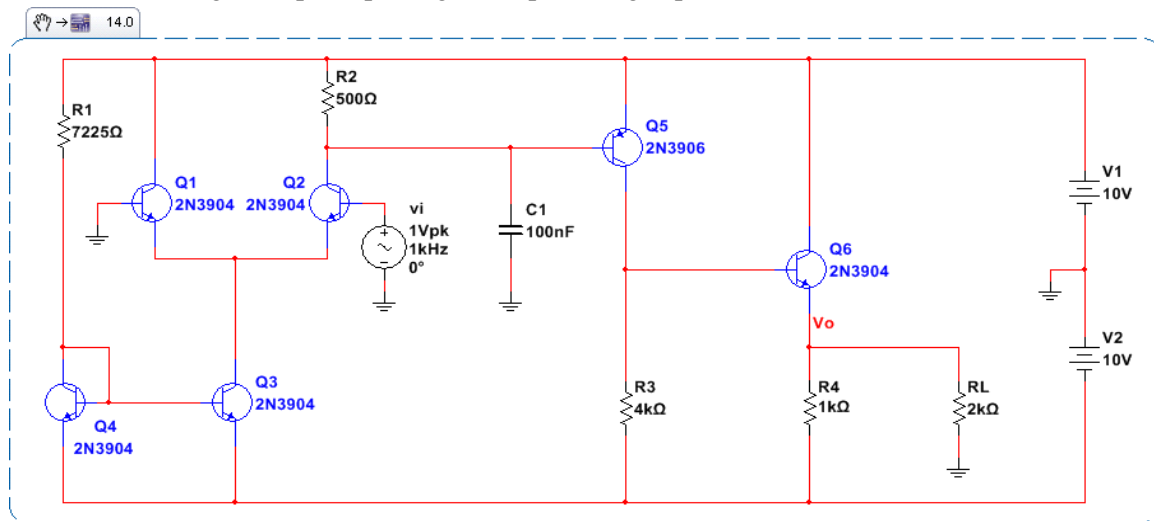


Figure 5: Moving the second pole using compensating capacitor

Problem 4 (continued): Stabilizing the Op-Amp using a Miller's capacitor


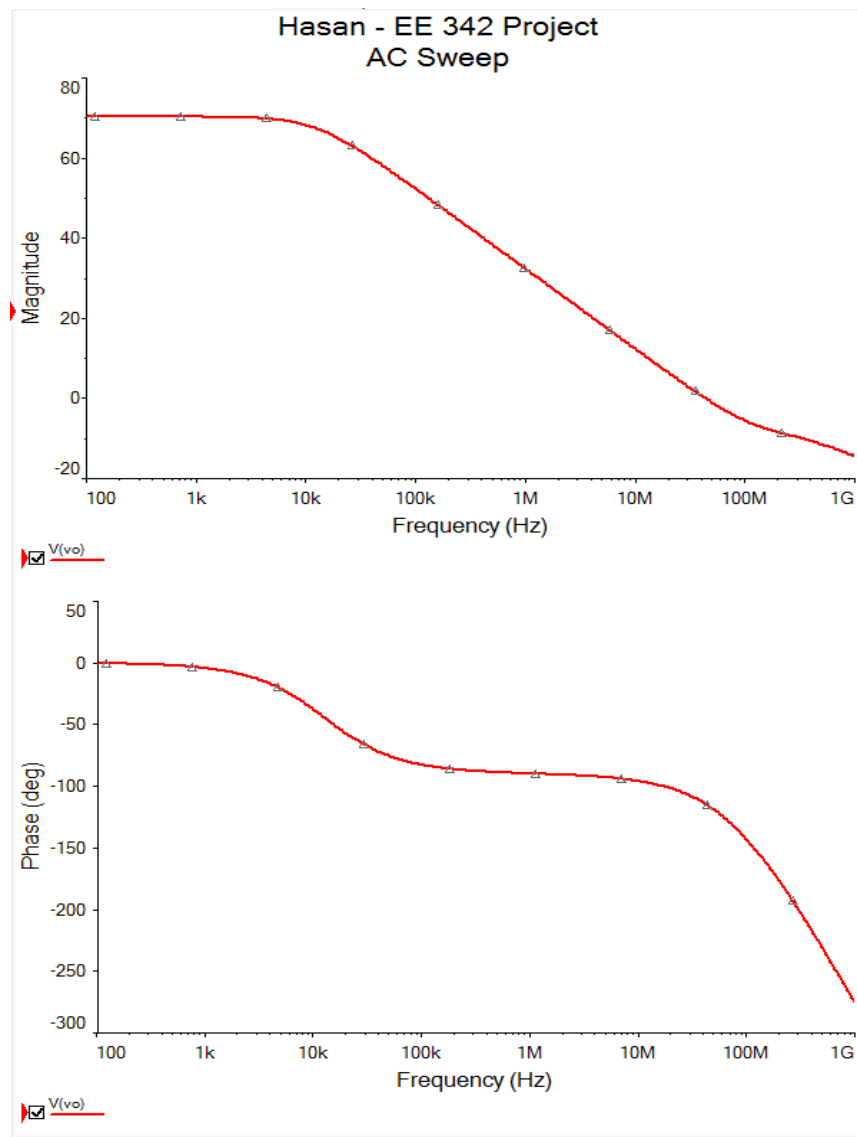
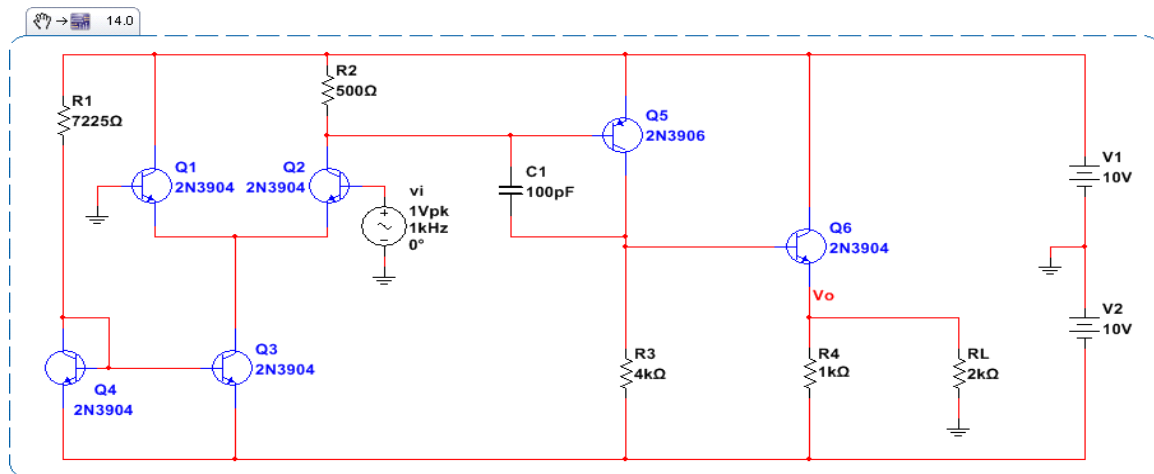
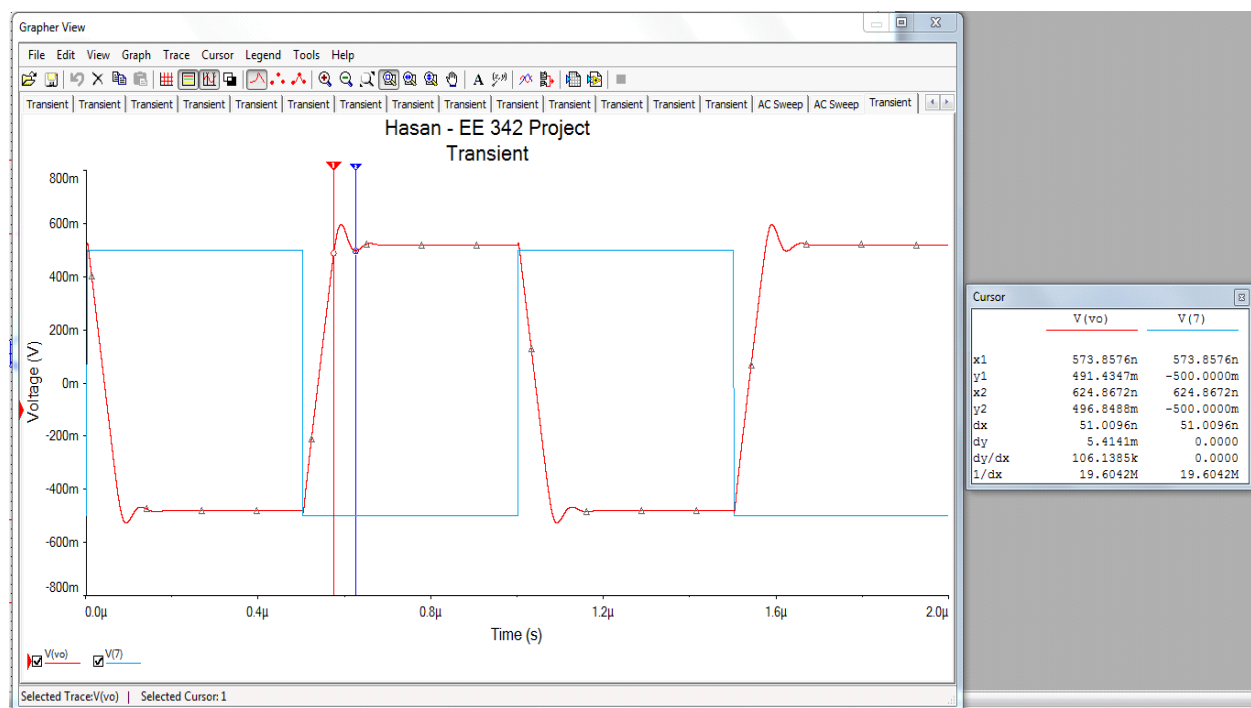


Figure 6: Moving the second pole using Miller's capacitor
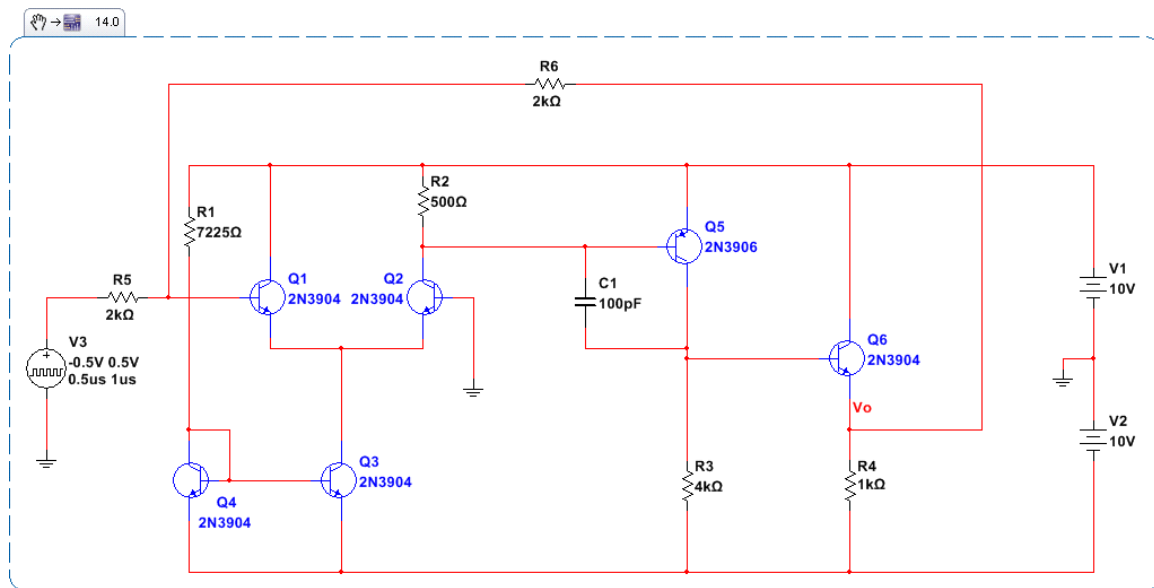
### Problem 5: Transient analysis of the frequency compensated Op-Amp



### Figure 7: Transient Analysis of the Op-Amp

**Calculations:**

Rise Time ~ 41.76 ns

Fall Time ~ 37.12 ns

Ringing Frequency  $\sim 1/51 \text{ ns} = 19.6 \text{ MHz}$

## Problem 6: AC simulation of the Op-Amp

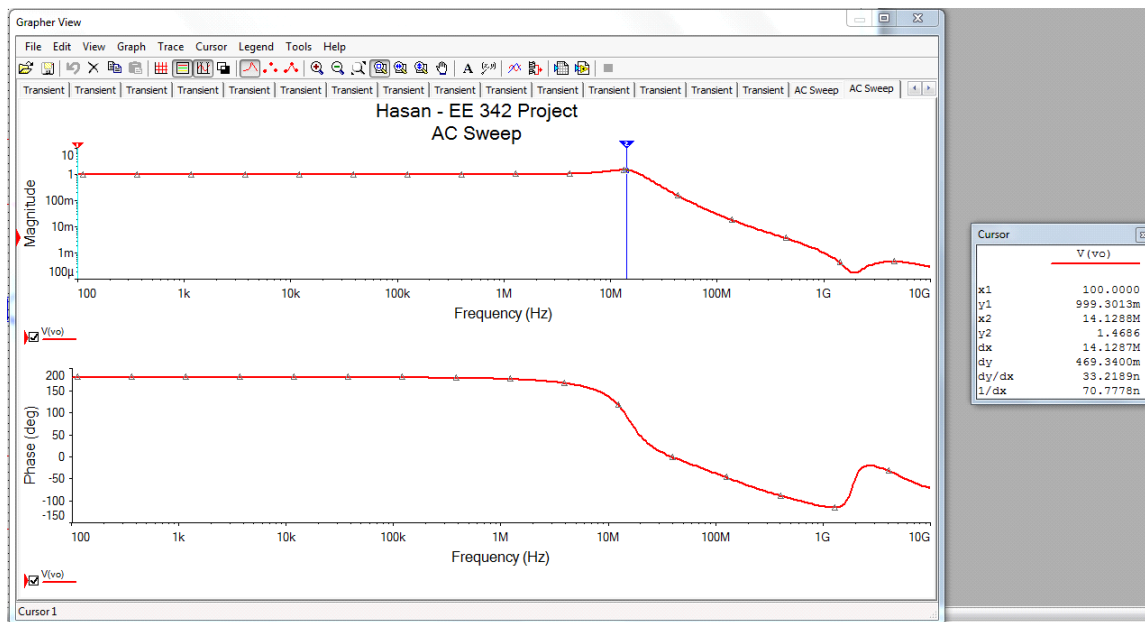


Figure 8: AC simulation of the Op-Amp

### Finding:

Yes, peaking was observed in the response of the Op-Amp. The peaking frequency was estimated to be around 14 MHz. This is very close to the observed ringing frequency of 19.6 MHz.